

## Computer-Aided VLSI System Design

### Homework 1: Arithmetic Logic Unit

TA: 李其祐 r11943123@ntu.edu.tw **Due Tuesday, Oct. 3<sup>rd</sup>, 13:59**

TA: 駱奕霖 f06943176@ntu.edu.tw

#### Data Preparation

- Decompress 1121\_hw1.tar with following command


```
tar -xvf 1121_hw1.tar
```

Files/Folder	Description
alu.v	Your design
testbench.v	File to test your design
pattern/	11 instruction tests for verification
01_run	NCverilog simulation command
02_lint	SpyGlass lint check
99_clean	Command for cleaning temporal files

#### Introduction

The Arithmetic logic unit (ALU) is one of the components of a computer processor. In this homework, you are going to design an ALU.

#### Block Diagram

 

## Specifications

1. Top module name: alu
2. Input/output description:

Signal Name	I/O	Width	Simple Description
<b>i_clk</b>	I	1	Clock signal in the system
<b>i_rst_n</b>	I	1	Active low asynchronous reset
<b>i_inst</b>	I	4	Instruction for ALU to operate
<b>i_data_a</b>	I	16	1. For instructions 0000~0100, signed input data with 2's complement representation (6-bit signed integer + 10-bit fraction) 2. For instructions 0101~0111, 16-bit number 3. For instructions 1000, 1001, Floating point (FP16)
<b>i_data_b</b>	I	16	
<b>o_valid</b>	O	1	Set <b>high</b> if ready to output result
<b>o_data</b>	O	16	1. For instructions 0000~0100, signed input data with 2's complement representation (6-bit signed integer + 10-bit fraction) 2. For instructions 0101~0111, 16-bit number 3. For instructions 1000, 1001, Floating point (FP16)
<b>o_busy</b>	O	1	Set <b>low</b> for one cycle, if ready for new input data. Set <b>high</b> , the input data remain unchanged.

3. All inputs are synchronized with the negative clock edge.
4. Active low asynchronous reset is used only once.
5. All outputs should be synchronized at clock rising edge (Flip-flops are added before outputs).
6. i\_data\_a, i\_data\_b and i\_inst will be sent while o\_busy is low.
7. o\_valid should be pulled high for only one cycle for each o\_data.
8. The testbed will get your output at negative clock edge and check the answer when your o\_valid is high.
9. You can raise the o\_valid at any moment.


## Design Description

- The followings are the functions of instructions you need to design for this homework:

<b>i_inst [3:0]</b>	<b>Operation</b>	<b>Description</b>
4'b0000	Signed Addition (FX)	$o\_data = i\_data\_a + i\_data\_b$
4'b0001	Signed Subtraction (FX)	$o\_data = i\_data\_a - i\_data\_b$
4'b0010	Signed Multiplication (FX)	$o\_data = i\_data\_a * i\_data\_b$
4'b0011	MAC	$o\_mult = i\_data\_a * i\_data\_b$ $o\_data_{new} = o\_mult + o\_data_{old}$
4'b0100	GELU	$o\_data = GELU(i\_data\_a)$
4'b0101	CLZ	Count leading zero bits
4'b0110	LRCW	Encode the CPOP result
4'b0111	LFSR	Generate pseudo random number
4'b1000	Signed Addition (FP)	$o\_data = i\_data\_a + i\_data\_b$
4'b1001	Signed Subtraction (FP)	$o\_data = i\_data\_a - i\_data\_b$

- Considerations between digital systems and signals:
  - For instruction 0011, you need to accumulate data with continuous MAC instructions (Multiply-accumulate first, then rounding and saturation).
  - For instructions I4, you need to implement a GELU function. To have an easier implementation, we approximate the GELU with tanh and use piecewise linear approximation to compute the tanh function. You can check 112-1\_HW1\_note.pdf for details.
  - For instructions I0~I4. If the output value exceeds the maximum value of 16b representation, use the maximum value as output, and vice versa.
  - For instructions I2~I4, the result needs to be rounded to the nearest number.
  - For instructions I5, only one input  $i\_data\_a$ .
  - For instruction I6, view  $i\_data\_a$  as the bit mask and  $i\_data\_b$  as the initial value
  - For instruction I7, view  $i\_data\_a$  as the initial value (seed) and  $i\_data\_b$  as the number of the iterations.
  - For instructions I8, I9, floating-point operations, remember to do rounding. You can check 112-1\_HW1\_note.pdf for details.

## Sample Waveform

 

## Submission

1. Create a folder named **studentID\_hw1** and follow the hierarchy below.

```
r11943123_hw1/
├── 01_RTL
│   ├── alu.v (and other verilog files)
│   ├── flist.v
│   └── rtl.f
```

Note: Use **lowercase** for the letter in your student ID. (Ex. r11943123\_hw1)

2. Compress the folder **studentID\_hw1** in a **tar file** named **studentID\_hw1\_vk.tar** (**k** is the number of version,  $k=1,2,\dots$ )

```
tar -cvf studentID_hw1_vk.tar studentID_hw1
```

TA will only check the last version of your homework.

Note:

- A. Use **lowercase** in your student ID. (Ex. r11943123\_hw1\_v1.tar)
  - B. Remember to put all the files in the studentID\_hw1
3. Submit to NTU Cool

## Grading Policy

---

1. TA will run your code with following format of command. Make sure to run this command with no error message.

```
vcs -f rtl.f -full64 -R -debug_access+all +v2k +define+$1
```

2. Pass all the instruction test to get full score.
  - Released pattern **70%**
    - I4, I8, I9: 8% for each instruction
    - I0~I3: 7 % for each instruction
    - I5~I7: 6% for each instruction
  - Hidden pattern **30%**
    - Only if you pass all patterns will you get the full 30% score.
    - I0~I3: 8000 (mix)
    - I4~I9: 2000 for each instruction
3. Spyglass check with **error (-20)**.
4. Do not use DesignWare for floating point operations.
5. **No late submission**
  - 0 point for this homework
6. Lose **5 points** for any wrong naming rule.

## References

---

1. Reference for fixed-point representation  
<https://www.allaboutcircuits.com/technical-articles/fixed-point-representation-the-q-format-and-addition-examples/>
2. Reference for rounding to the nearest  
<https://www.mathworks.com/help/fixedpoint/ug/rounding.html>
3. Reference for FP16 representation  
[https://en.wikipedia.org/wiki/Half-precision\\_floating-point\\_format](https://en.wikipedia.org/wiki/Half-precision_floating-point_format)
4. CMU Lecture – Floating point  
<https://www.cs.cmu.edu/afs/cs/academic/class/15213-s16/www/lectures/04-float.pdf>