


Computer-Aided VLSI System Design

Homework 2: Simple MIPS CPU

Graduate Institute of Electronics Engineering, National Taiwan University




NTU GIEE

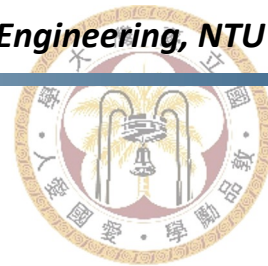

Goal

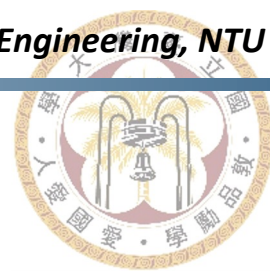- In this homework, you will learn
 - How to write testbench
 - How to design FSM
 - How to use IP
 - Generate patterns for testing





Introduction

- Central Processing Unit (CPU) is the important core in the computer system. In this homework, you are asked to design a simple MIPS CPU, which contains the basic module of program counter, ALU and register files. The instruction set of the simple CPU is similar to MIPS structure.


Instruction set

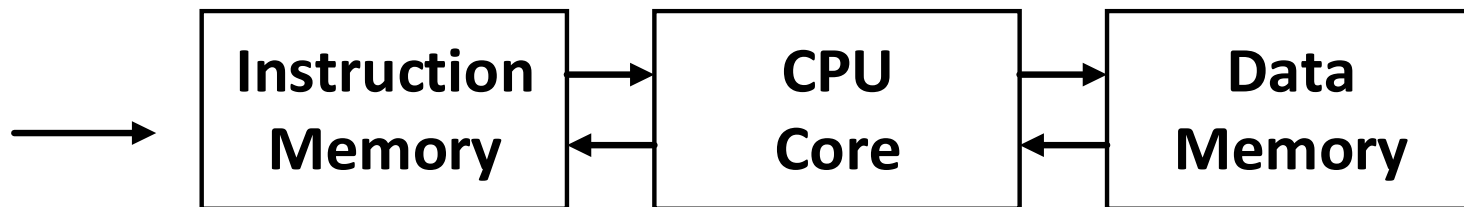
```
addi $7 $3 4
sub  $7 $7 $5
sw   $7 $4 8
bne  $3 $5 12
lw   $6 $0 8
add  $7 $6 $2
sw   $7 $4 8
eof
```



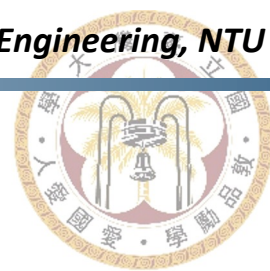


Block Diagram

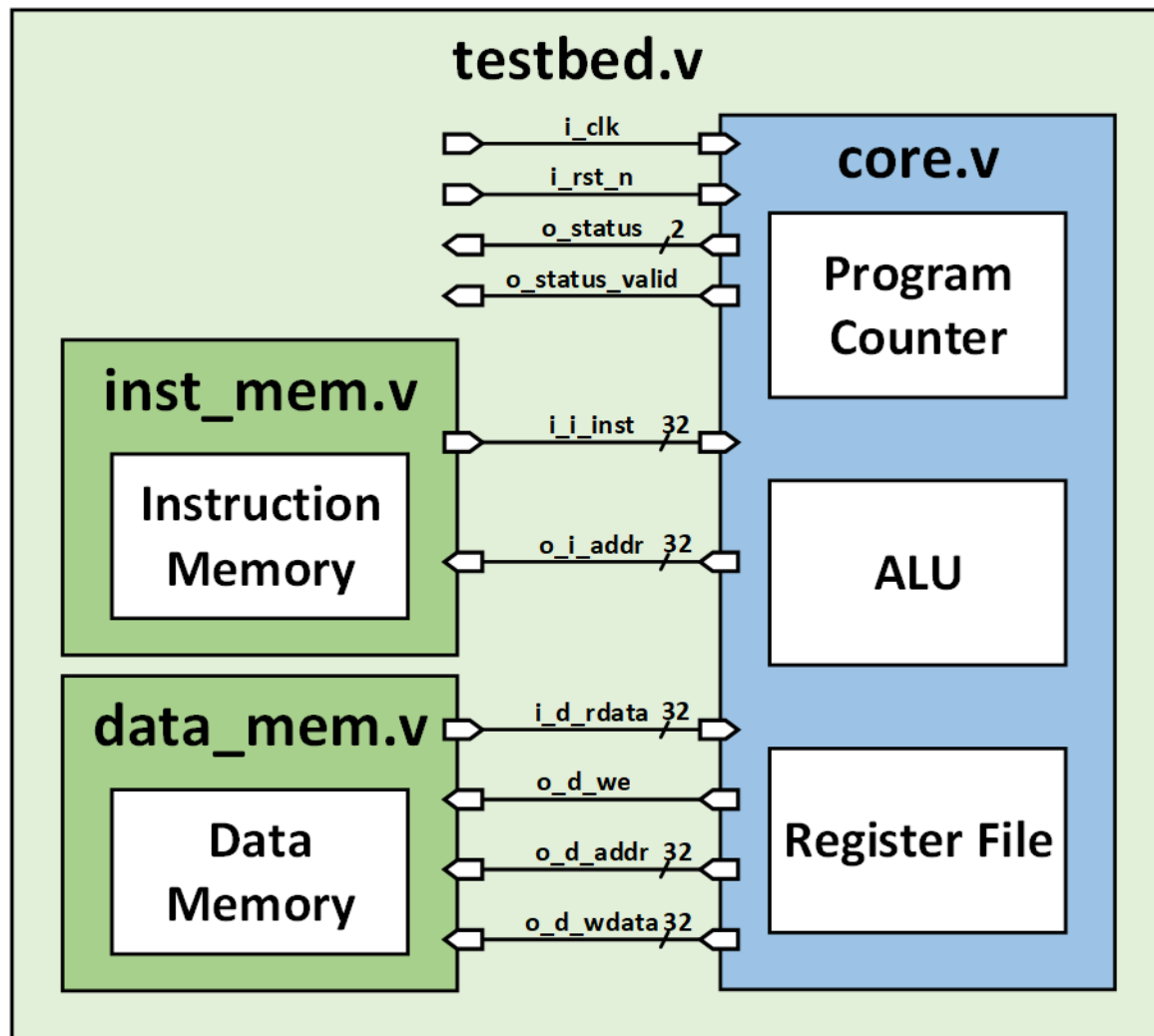

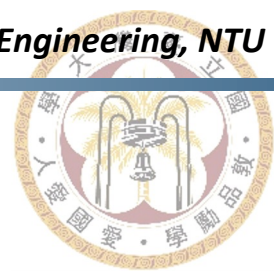


Input/Output

Signal Name	I/O	Width	Simple Description
i_clk	I	1	Clock signal in the system.
i_rst_n	I	1	Active low asynchronous reset.
o_i_addr	O	32	Address from program counter (PC)
i_i_inst	I	32	Instruction from instruction memory
o_d_we	O	1	Write enable of data memory Set low for reading mode, and high for writing mode
o_d_addr	O	32	Address for data memory
o_d_wdata	O	32	Unsigned data input to data memory
i_d_rdata	I	32	Unsigned data output from data memory
o_status	O	2	Status of core processing to each instruction
o_status_valid	O	1	Set high if ready to output status

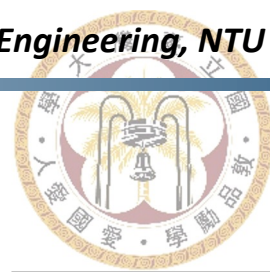


Specification

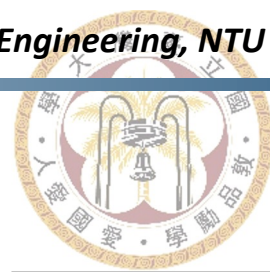- All outputs should be synchronized at clock **rising** edge.
- Instruction memory and data memory are provided. All values in memory are reset to be zero.
- You should create **32 unsigned 32-bit registers** in register file.
- Less than **1024** instructions are provided for each pattern.
- The whole processing time can't exceed **120000** cycles.




Specification

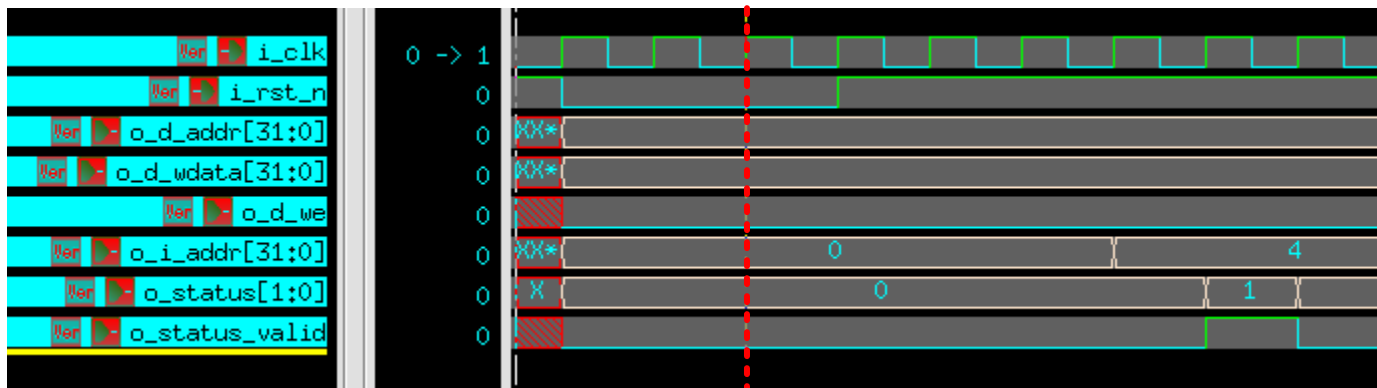- You should set all your outputs and register file to be zero when `i_rst_n` is **low**. Active low asynchronous reset is used.




All outputs must be 0



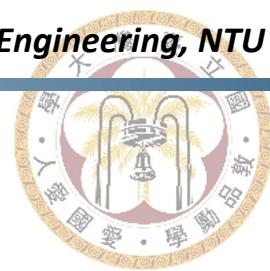


Specification

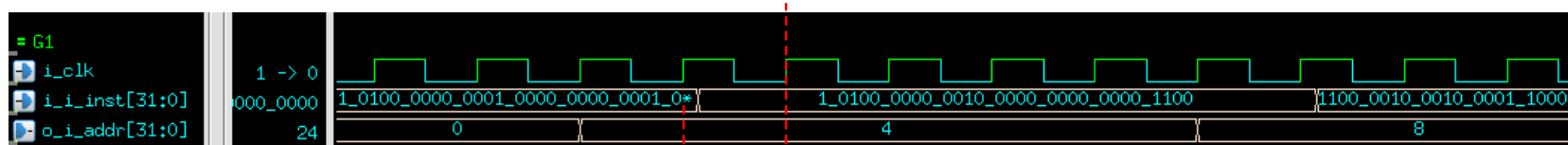- After outputting `o_i_addr` to instruction memory, the core can receive the corresponding `i_i_inst` at the next rising edge of the clock.




Output `o_i_addr` for relative instruction →

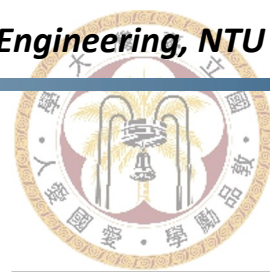← Get `i_i_inst` at the next rising edge of clock




Specification

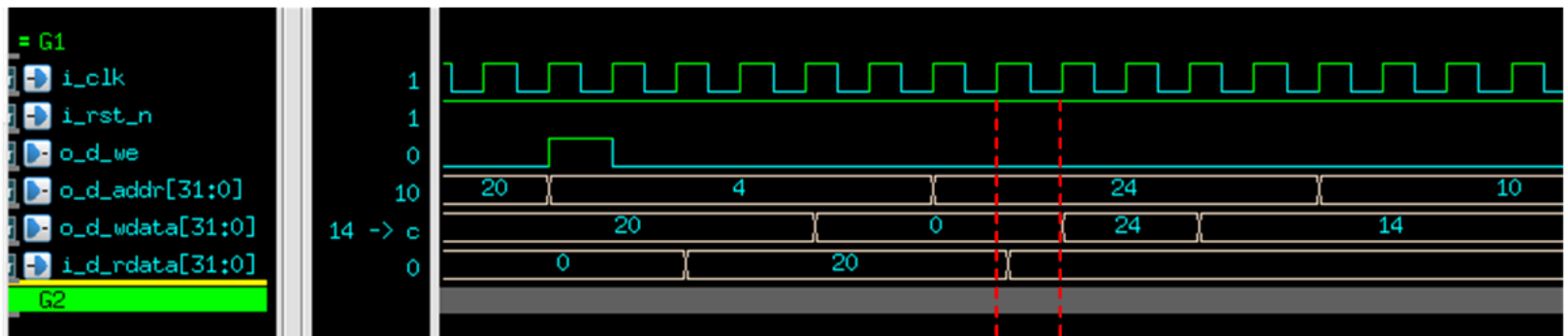- To load data from the data memory, set `o_d_we` to **0** and `o_d_addr` to relative address value. `i_d_rdata` can be received at the next rising edge of the clock.




`o_d_we` = 0, load data from data memory at `o_d_addr` = 24

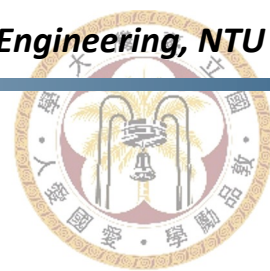Receive `i_d_rdata` at next rising edge of clock




Specification

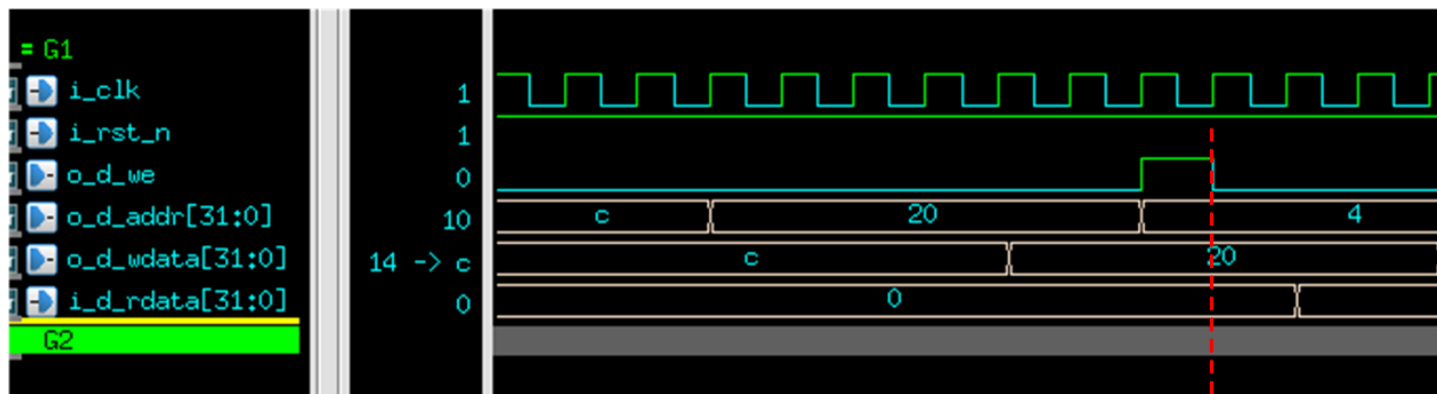- To save data to the data memory, set `o_d_we` to **1**, `o_d_addr` to relative address value, and `o_d_wdata` to the written data.




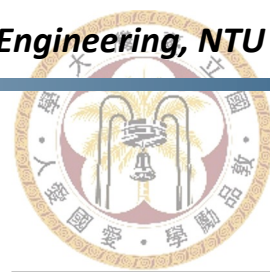**`o_d_we` = 1, store `o_d_wdata`
to data memory at `o_d_addr` = 4**




Specification

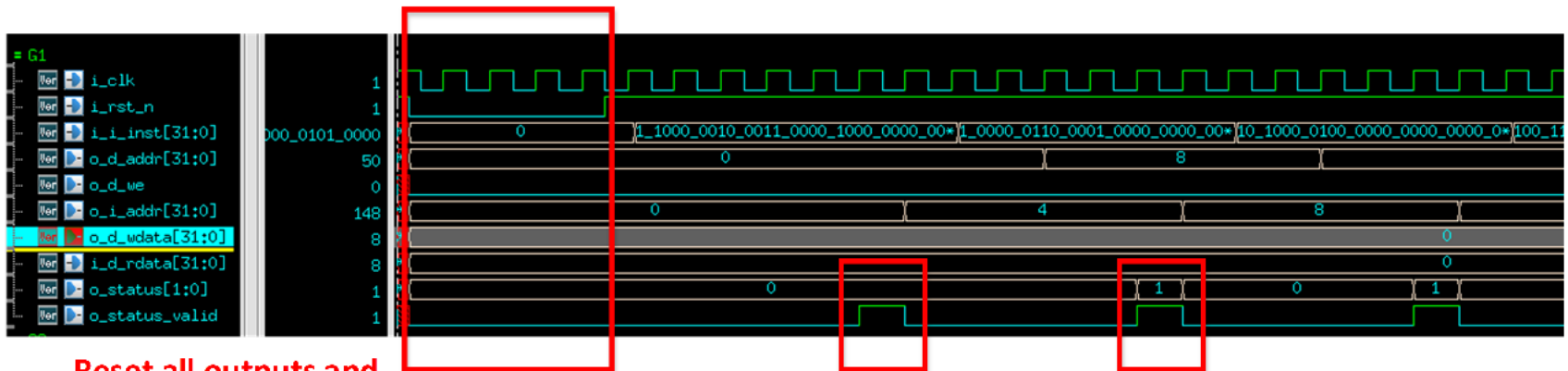- Your `o_status_valid` should be turned to **high** for only **one cycle** for every `o_status`.
- The testbench will get your output at negative clock edge to check the `o_status` if your `o_status_valid` is **high**.




Reset all outputs and register file to 0

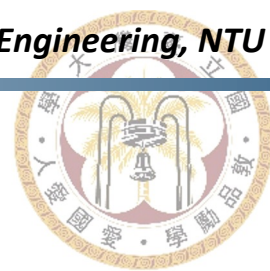
`o_status` is 0 if R-type instruction success,
`o_status` is 1 if I-type instruction success



Specification

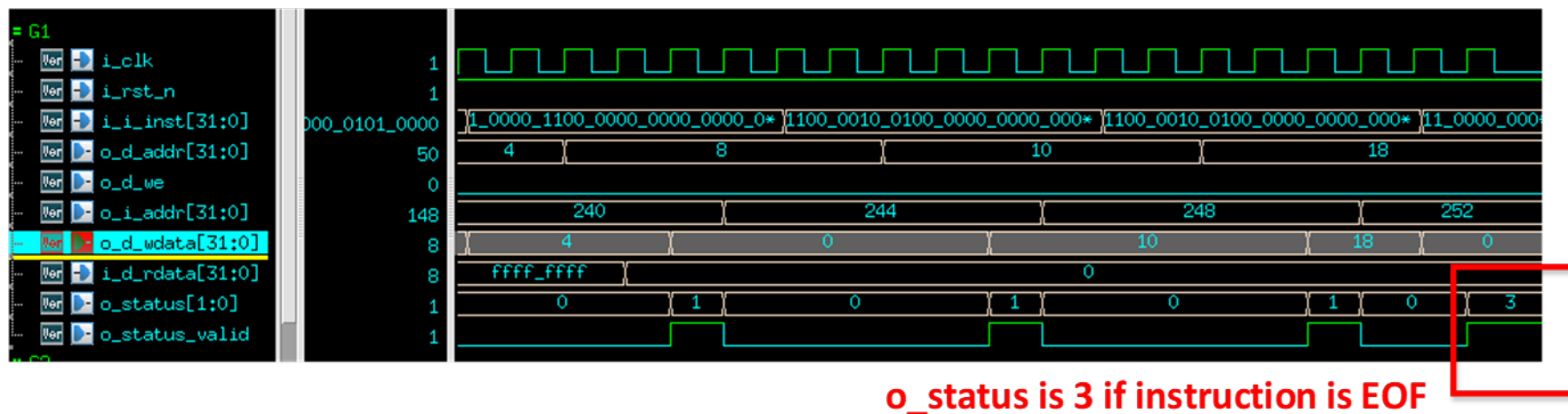
- When you set o_status_valid to **high** and o_status to **3**, stop processing. The testbench will check your data memory value with golden data.



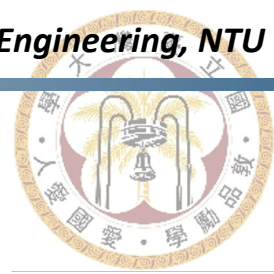


Specification

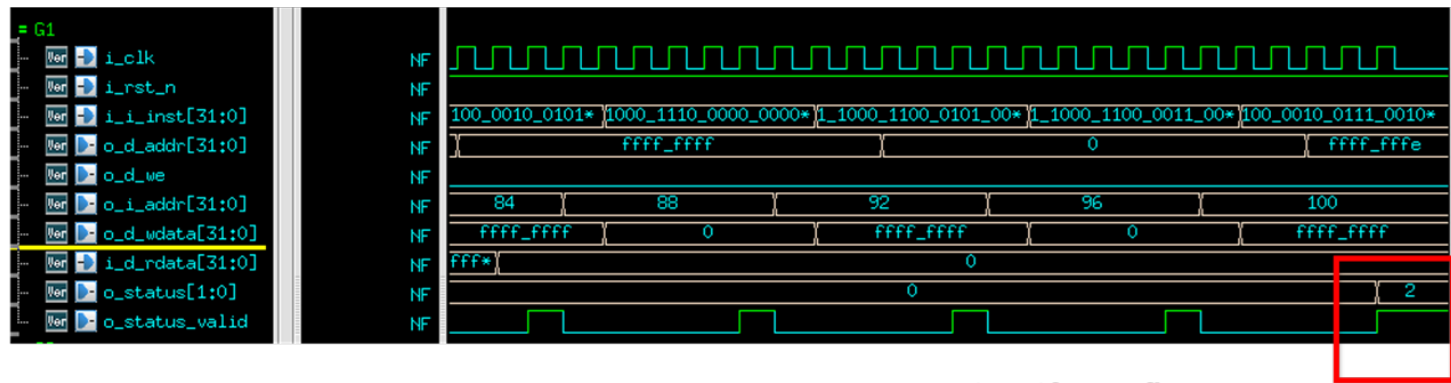- If overflow happened, stop processing and raise o_status_valid to **high** and set o_status to **2**. The testbench will check your data memory value with golden data.




o_status is 2 if overflow occur

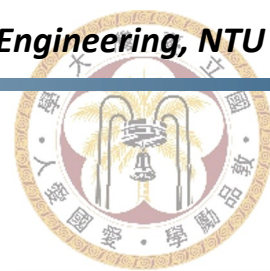


Program Counter

- Program counter is used to control the address of instruction memory.

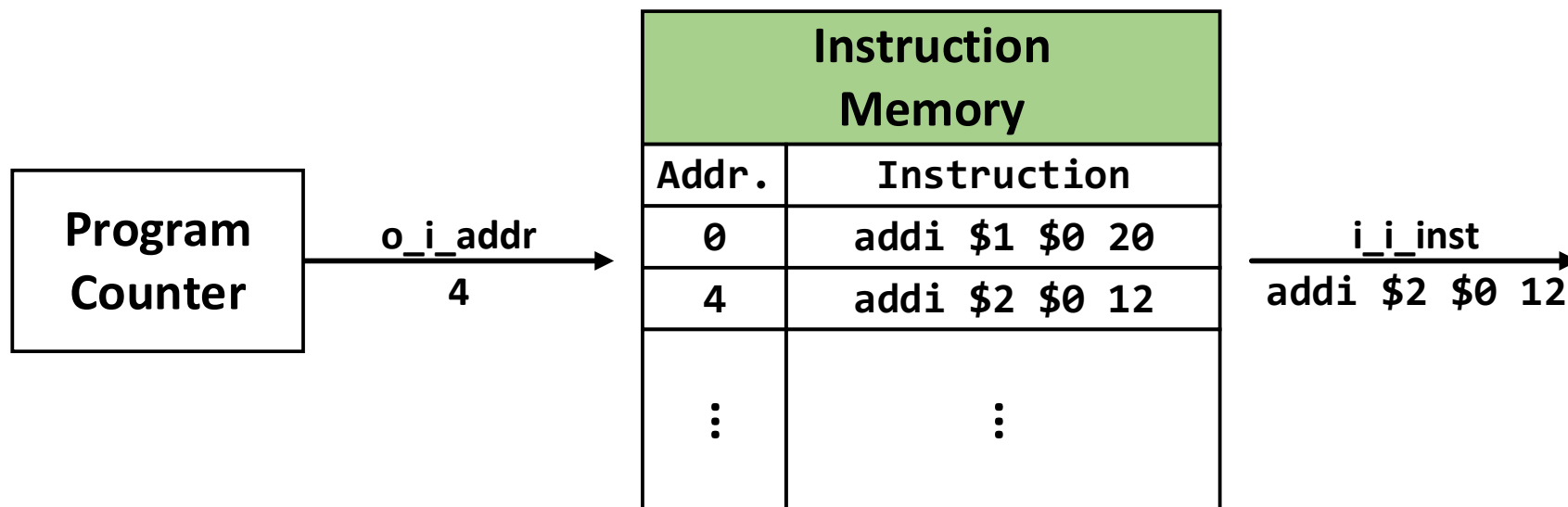
$\$pc = \$pc + 4$ for every instruction (except **beq**, **bne**)



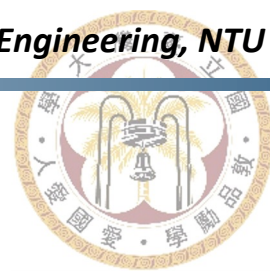


Instruction mapping


▪ R-type

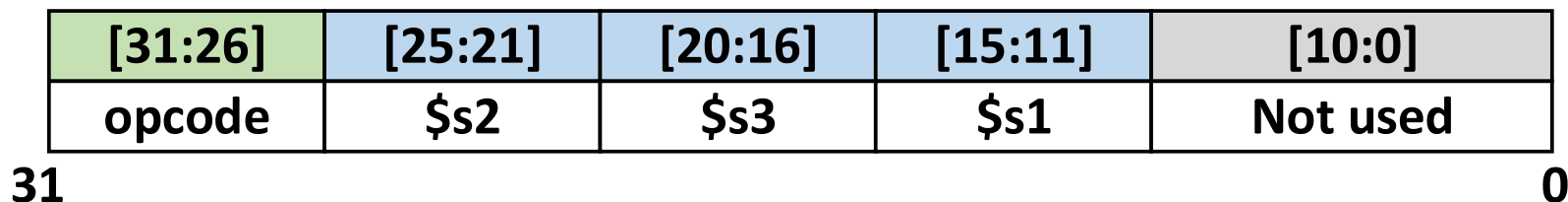


▪ I-type

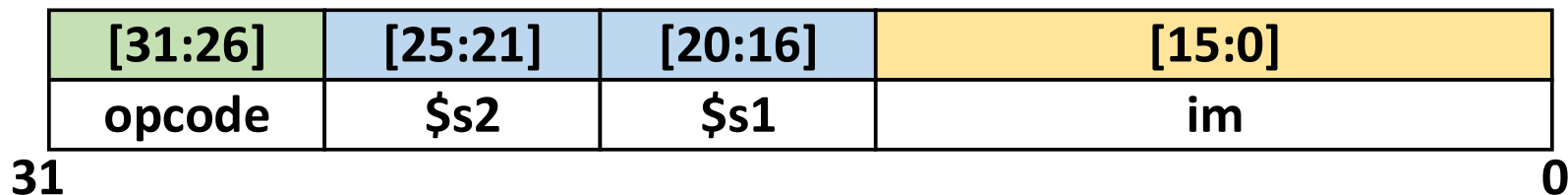


▪ EOF

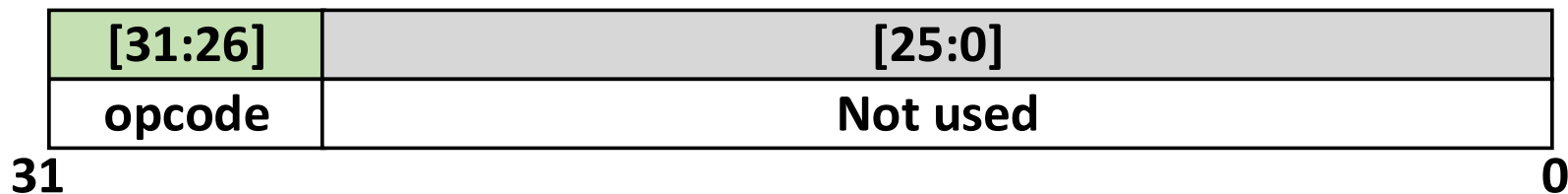

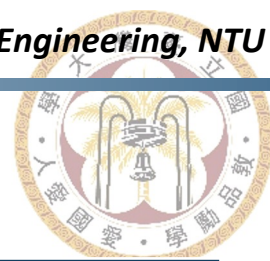

Instruction

Operation	Assemble	Opcode	Type	Meaning	Note
Add (integer)	add	6'd1	R	$\$s1 = \$s2 + \$s3$	Signed Operation
Subtract (integer)	sub	6'd2	R	$\$s1 = \$s2 - \$s3$	Signed Operation
Multiply (integer)	mul	6'd3	R	$\$s1 = \$s2 * \$s3$	Signed Operation
Add (floating point)	fp_add	6'd13	R	$\$s1 = \$s2 + \$s3$	Floating Point Operation
Subtract (floating point)	fp_sub	6'd14	R	$\$s1 = \$s2 - \$s3$	Floating Point Operation
Multiply (floating point)	fp_mul	6'd15	R	$\$s1 = \$s2 * \$s3$	Floating Point Operation
Add immediate	addi	6'd4	I	$\$s1 = \$s2 + im$	Signed Operation
Load word	lw	6'd5	I	$\$s1 = \text{Mem}[\$s2 + im]$	Signed Operation
Store word	sw	6'd6	I	$\text{Mem}[\$s2 + im] = \$s1$	Signed Operation

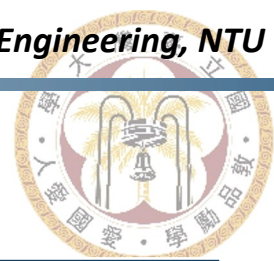


Instruction (cont'd)

Operation	Assemble	Opcode	Type	Meaning	Note
AND	and	6'd7	R	$\$s1 = \$s2 \& \$s3$	Bit-wise
OR	or	6'd8	R	$\$s1 = \$s2 \mid \$s3$	Bit-wise
NOR	nor	6'd9	R	$\$s1 = \sim(\$s2 \mid \$s3)$	Bit-wise
Branch on equal	beq	6'd10	I	if($\$s1 == \$s2$), $\$pc = \$pc + im$; else, $\$pc = \$pc + 4$	PC-relative Unsigned Operation
Branch on not equal	bne	6'd11	I	if($\$s1 \neq \$s2$), $\$pc = \$pc + im$; else, $\$pc = \$pc + 4$	PC-relative Unsigned Operation
Set on less than	slt	6'd12	R	if($\$s2 < \$s3$), $\$s1 = 1$; else, $\$s1 = 0$	Signed Operation
Shift left logical	sll	6'd16	R	$\$s1 = \$s2 \ll \$s3$	Unsigned Operation
Shift right logical	srl	6'd17	R	$\$s1 = \$s2 \gg \$s3$	Unsigned Operation
End of File	eof	6'd18	EOF	Stop processing	Last instruction in the pattern

Note: The notation of **im** in I-type instruction is **2's complement**.

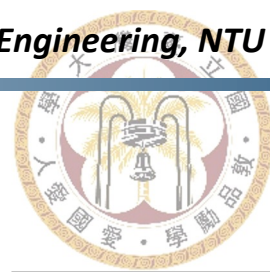Note: Signed operations indicates that the data in register file are expressed in **2's complement**.




Floating Point

- For instructions **fp_add**, **fp_sub**, **fp_mul**, you will have to implement operations with **floating point** format
- Only normal numbers will be provided in test patterns
 - You do not need to consider infinity, denormalized numbers, and NaN
- IEEE 754 single precision format [1]
 - Round to nearest even [2]




31

0

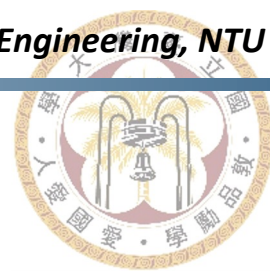

Floating Point


Rounding

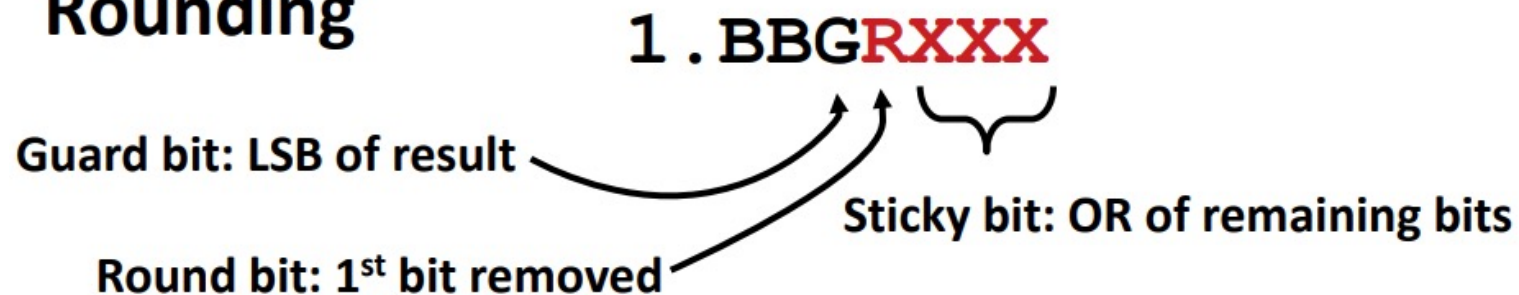

■ Round up conditions

- Round = 1, Sticky = 1 \rightarrow > 0.5
- Guard = 1, Round = 1, Sticky = 0 \rightarrow Round to even

<i>Value</i>	<i>Fraction</i>	<i>GRS</i>	<i>Incr?</i>	<i>Rounded</i>
128	1.000 0000	000	N	1.000
15	1.101 0000	100	N	1.101
17	1.000 1000	010	N	1.000
19	1.001 1000	110	Y	1.010
138	1.000 1010	011	Y	1.001
63	1.111 1100	111	Y	10.000

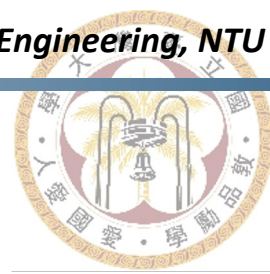


Memory IP

- Instruction memory
 - Size: 1024×32 bit
 - `i_addr[11:2]` for address mapping in instruction memory
- Data memory
 - Size: 64×32 bit
 - `i_addr[7:2]` for address mapping in data memory

```
module inst_mem (  
    input          i_clk,      // 1-bit  
    input          i_rst_n,    // 1-bit  
    input [ 31 : 0 ] i_addr,    // 32-bit  
    output [ 31 : 0 ] o_inst    // 32-bit  
);
```

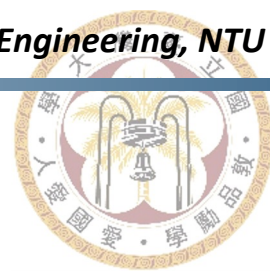
```
module data_mem (  
    input          i_clk,  
    input          i_rst_n,  
    input          i_we,  
    input [ 31 : 0 ] i_addr,  
    input [ 31 : 0 ] i_wdata,  
    output [ 31 : 0 ] o_rdata  
);
```



Status


- 4 statuses of o_status

o_status[1:0]	Definition
2'd0	R_TYPE_SUCCESS
2'd1	I_TYPE_SUCCESS
2'd2	MIPS_OVERFLOW
2'd3	MIPS_END

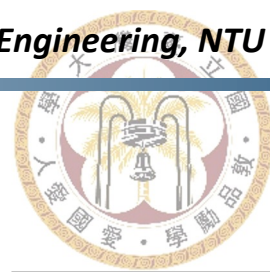

Overflow

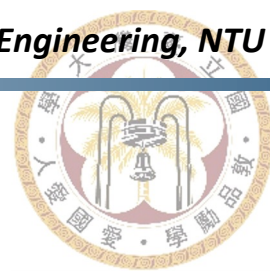
- Overflow may be happened.
 - **Situation1**: Overflow happened at arithmetic instructions (add, sub, mul, addi)
 - **Situation2**: If output address are mapped to unknown address in data/instruction memory. (Do not consider the case if instruction address is beyond eof, but the address mapping is in the size of instruction memory)



rtl.f

- Filelist
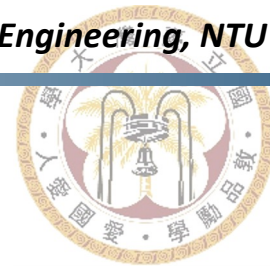
```
// -----  
// Simulation: HW2 simple mips CPU  
// -----  
  
// define files  
// -----  
../00_TESTBED/define.v  
  
// testbench  
// -----  
../00_TESTBED/testbed.v  
../00_TESTBED/inst_mem.vp  
../00_TESTBED/data_mem.vp  
  
// design files  
// -----  
./core.v
```




core.v

- Do not modify interface

```
module core #( // DO NOT MODIFY!!!
    parameter ADDR_WIDTH = 32,
    parameter INST_WIDTH = 32,
    parameter DATA_WIDTH = 32
) (
    input                i_clk,
    input                i_rst_n,
    output [ADDR_WIDTH-1:0] o_i_addr,
    input  [ADDR_WIDTH-1:0] i_i_inst,
    output                o_d_we,
    output [ADDR_WIDTH-1:0] o_d_addr,
    output [DATA_WIDTH-1:0] o_d_wdata,
    input  [DATA_WIDTH-1:0] i_d_rdata,
    output [                1:0] o_status,
    output                o_status_valid
);


endmodule
```

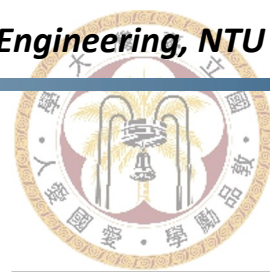define.v

```
// opcode definition
`define OP_ADD      1
`define OP_SUB      2
`define OP_MUL      3
`define OP_ADDI     4
`define OP_LW       5
`define OP_SW       6
`define OP_AND      7
`define OP_OR       8
`define OP_NOR      9
`define OP_BEQ     10
`define OP_BNE     11
`define OP_SLT     12
`define OP_FP_ADD  13
`define OP_FP_SUB  14
`define OP_FP_MUL  15
`define OP_SLL     16
`define OP_SRL     17
`define OP_EOF     18

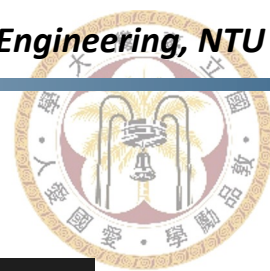// MIPS status definition
`define R_TYPE_SUCCESS 0
`define I_TYPE_SUCCESS 1
`define MIPS_OVERFLOW 2
`define MIPS_END 3
```



testbed_temp.v

- Things to add in your testbench
 - Clock
 - Reset
 - Waveform file
 - Function test
 - ...


```
module testbed;

    reg clk = 0;
    reg rst_n = 1;
    wire [ 31 : 0 ] imem_addr;
    wire [ 31 : 0 ] imem_inst;
    wire            dmem_we;
    wire [ 31 : 0 ] dmem_addr;
    wire [ 31 : 0 ] dmem_wdata;
    wire [ 31 : 0 ] dmem_rdata;
    wire [ 1 : 0 ] mips_status;
    wire            mips_status_valid;
```

```
    core u_core (
        .i_clk(),
        .i_rst_n(),
        .o_i_addr(),
        .i_i_inst(),
        .o_d_we(),
        .o_d_addr(),
        .o_d_wdata(),
        .i_d_rdata(),
        .o_status(),
        .o_status_valid()
    );

    inst_mem u_inst_mem (
        .i_clk(),
        .i_rst_n(),
        .i_addr(),
        .o_inst()
    );

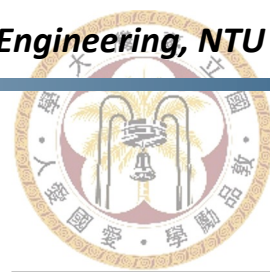    data_mem u_data_mem (
        .i_clk(),
        .i_rst_n(),
        .i_we(),
        .i_addr(),
        .i_wdata(),
        .o_rdata()
    );
```




Protected Files

- The following files are protected
 - inst_mem.vp
 - data_mem.vp

```
module inst_mem (
    input          i_clk,
    input          i_rst_n,
    input [ 31 : 0 ] i_addr,
    output [ 31 : 0 ] o_inst
);
`protected
Nd15kSQH5DT^<D9i:i7T7ceFn3@o:C2]Ke:L;dfq^QGQOG?3K:ogIe8]1ge<gcg3
lCH3E]ekmLN<RVkKa1o39E7E21a;`hJRSFMUb2pAgL?TeZdH>]^RK;KWYU@>G2G6
H[IMYG;D<[Z>;0`?NbPoEAQM<_ZfDbp1HN@HmqS0`Q<5[53C:9UD4^:Y44]9a^e
PDH[cdHb;HPi\R4k7mAlPdY8ZpI=4?nNZgQ2I>QUg[agM4j@cTl]hnMoC<i1F9DR
[kf;]ULlecpF`H;9L2DeZa>@LdfLgfb8l4bwgT:_P3?ENhifQW@_Ne;gMZE9@f0A
OERY:F4d68KqAIn]N1dj4LN7_8:Uigk?9UJ9JYQM4l=Lq\TEXDQ01>Zo^SJq=Cge
?kp68am:9p81Q1[<jSXm?;GhoPHYKp\Q][2epXn_18k8LA5g=N7=D?=VOX<Ham8
[A:Qc;Rlp038>d9_Qk9cfk?:5hXP>LT3n=DP08A_]wPa6nA3cYZjG132qB9]I4kp
>=:4m9P`dCB8@?ip`@VR7AahIggjNR:M1:_\KXE1BF0m<Bb@ZS[^W7EheJ18mX8;
?7F`Pg\CCA8igfFUoWY@k>Yq=U3_4>E50_nJ\`aUGcfWD_89dab]cUQFF<?2P?OG
qWglWC[\iqnjC<OipHHnb<T4Sg<:UORVSVocI_g?<a@o__<PQ493cZIE;7^Sp1AQ
G<c17[ ]R\>VT]]LA\7?Uk=]\bG19MT9N;K<Y92[iK0ged92EIkQZliw>q1G]QI?5
ST06RFN<KJl@VM1EWKSmb1B5U:BaX`E7of7mq0JBg0`9k$
`endprotected

endmodule
```

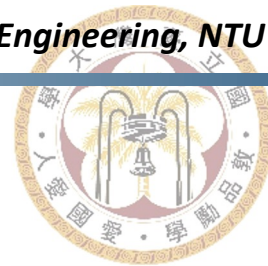


Command

- 01_run
 - Usage: ./01_run p0

```
vcs -f rtl.f -full64 -R -debug_access+all  
+define+$1 +v2k
```

- 99_clean_up
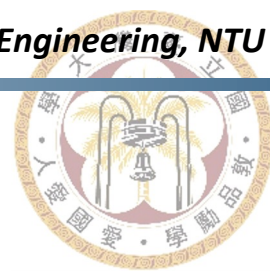
```
rm -rf *.history *.key *.log  
rm -rf novas.rc novas.fsdb novas.conf  
rm -rf INCA_libs nWaveLog BSSLib.lib++
```




PATTERN

- Files in PATTERN are for your references

inst_assemble.dat

```
-----  
R-type  $s2  $s3  $s1  
I-type  $s2  $s1  im  
-----
```
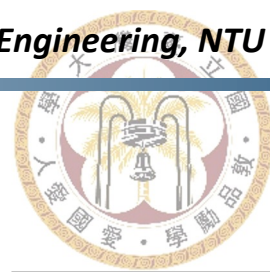
```
and      $1    $3    $1  
lw       $3    $1     8  
bne      $2    $0     8  
add      $7    $1    $4  
slt      $6    $5    $4  
slt      $4    $1    $1  
lw       $1    $3   12  
lw       $7    $7     4  
bne      $6    $7     8  
lw       $6    $5     8  
lw       $5    $2     8
```




Grading Policy

- TA will run your code with following command

```
vcs -f rtl.f -full64 -R -debug_access+all  
+define+p0 +v2k
```

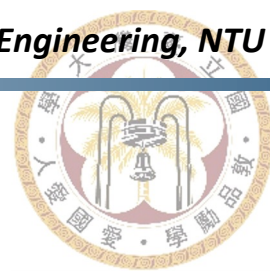- Pass the patterns to get full score
 - Provided pattern: **70%**
 - **30%** for each test (data from data memory: **15%**, status check: **15%**)
 - **10%** for spyglass check
 - Hidden pattern: **30%** (20 patterns in total)
 - **1.5%** for each test (data & status both correct)
- **No delay submission is allowed**
- Lose **5 point** for any wrong naming rule or format for submission




Submission

- Create a folder named **studentID_hw2**, and put all below files into the folder


```
r11943133_hw2
├── 01_RTL
│   ├── rtl.f (your file list)
│   ├── core.v
│   ├── flist.v (your file list for lint check)
│   └── all other design files (optional)
```

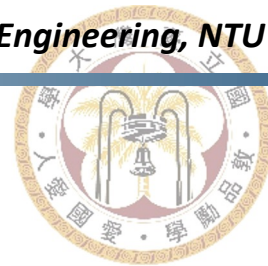- Compress the folder **studentID_hw2** in a tar file named **studentID_hw2_vk.tar** (k is the number of version, $k = 1, 2, \dots$)
 - Use lower case for student ID. (Ex. r11943133_hw2_v1.tar)
- Submit to NTU Cool



Hint

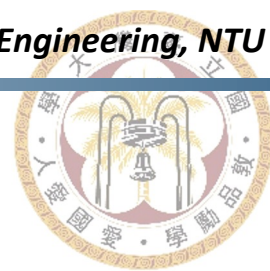- Design your FSM with following states
 1. Idle
 2. Instruction Fetching
 3. Instruction decoding
 4. ALU computing/ Load data
 5. Data write-back
 6. Next PC generation
 7. Process end



Reference

- [1] IEEE 754 Single Precision Format
 - https://zh.wikipedia.org/zh-tw/IEEE_754
- [2] Round to Nearest Even
 - <https://www.cs.cmu.edu/afs/cs/academic/class/15213-s16/www/lectures/04-float.pdf>